

# **BASIC ELECTRONICS ENGINEERING**

**(RBL1B002)**

## ***MODULE-1***

# **BJT DC BIASING**

- 4 types of biasing circuits are there.
  - Fixed Bias Circuit
  - Emitter Stabilized Bias Circuit
  - Voltage Divider Bias Circuit
  - DC bias with voltage feedback

## **NOTE:**

$$1. I_E = I_B + I_C$$


$$2. \beta = \frac{I_C}{I_B}$$

$$3. I_E \approx I_C$$

$$4. V_{BE} = \begin{cases} 0.7 \text{ for Si} \\ 0.3 \text{ for Ge} \end{cases}$$

$$5. V_{XY} = V_X - V_Y$$

# Voltage Divider Bias Circuit

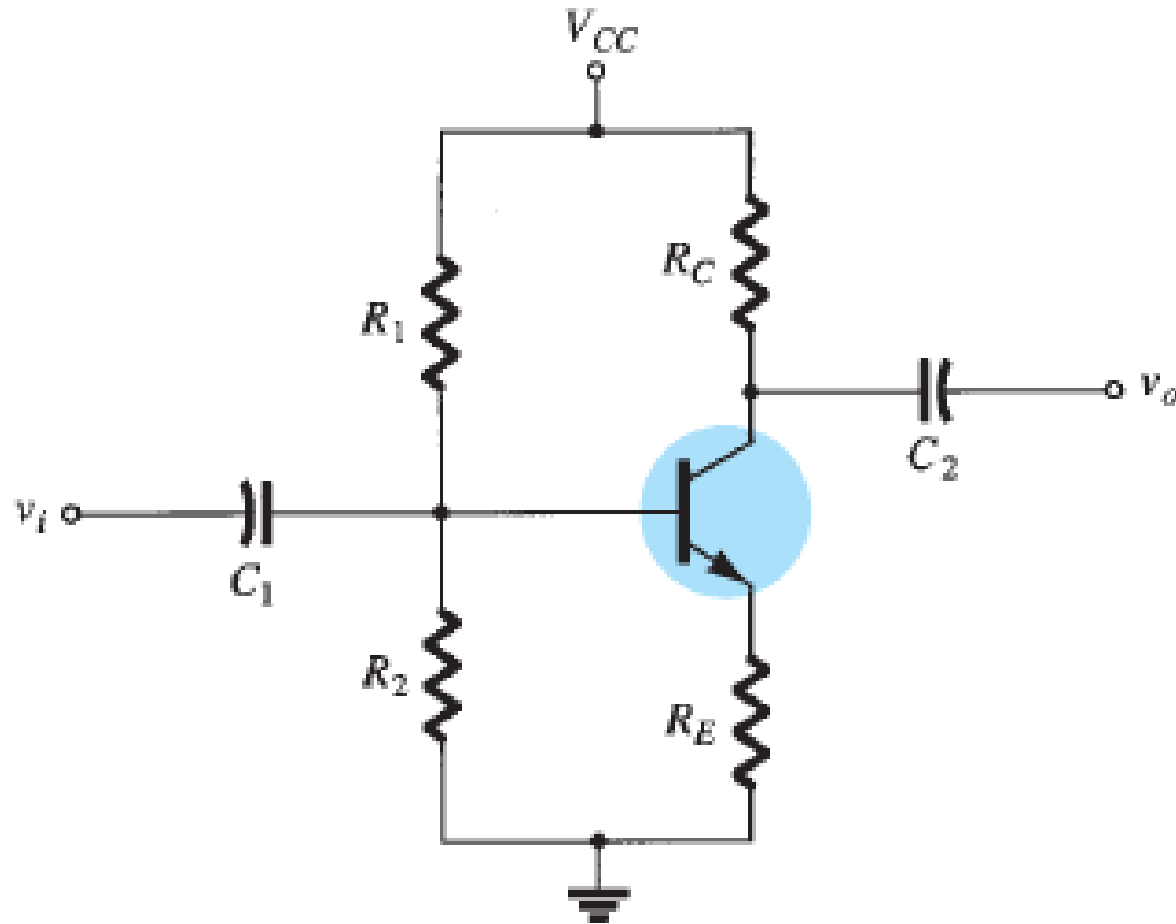

# Voltage Divider Bias Circuit

- In the previous bias configurations, the bias current  $I_{CQ}$  and voltage  $V_{CEQ}$  at Q point were a function of the current gain ( $\beta$ ) of the transistor.
- Since  $\beta$  is temperature sensitive it is desirable to develop a bias circuit that is independent of transistor  $\beta$  or less dependent on  $\beta$ .
- The Voltage divider bias configuration provides such type of network.
- If the circuit parameters are properly chosen the resulting levels of  $I_{CQ}$  and  $V_{CEQ}$  can be almost totally independent of  $\beta$ .

# Voltage Divider Bias Circuit

There are two methods that can be applied to analyse the voltage divider configuration.

- 1) Exact Analysis

- 2) Approximate Analysis


The exact analysis can be applied to any voltage divider configuration.

But the approximate method can be applied only if some specific conditions are satisfied.

# Voltage Divider Bias Circuit
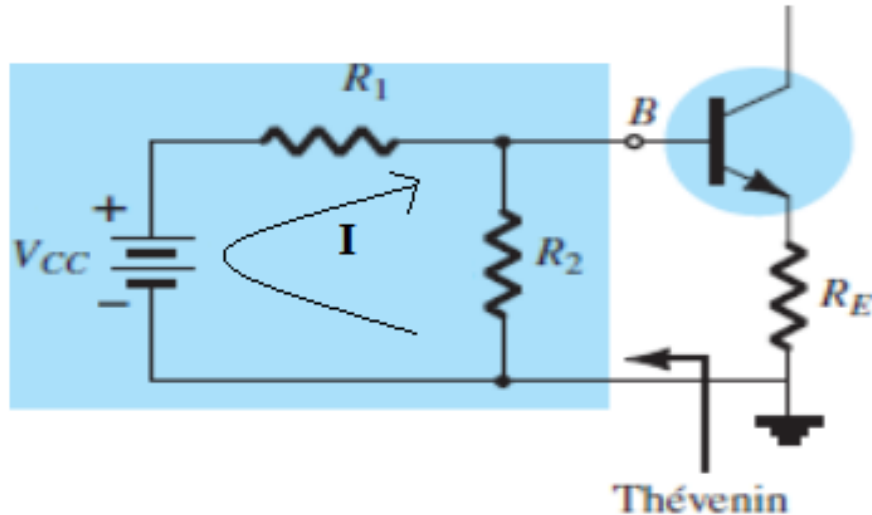
## EXACT Analysis:

The BE junction of the voltage divider bias circuit can be redrawn as



# Voltage Divider Bias Circuit

Assuming the current  $I$ , by KVL

$$V_{CC} - IR_1 - IR_2 = 0$$


$$\Rightarrow I = \frac{V_{CC}}{R_1 + R_2}$$

Hence the voltage across  $R_2$  i.e. thevenin's voltage is given by

$$E_{Th} = I \times R_2 = \frac{R_2 V_{CC}}{R_1 + R_2}$$

And the thevenin's resistance is given by

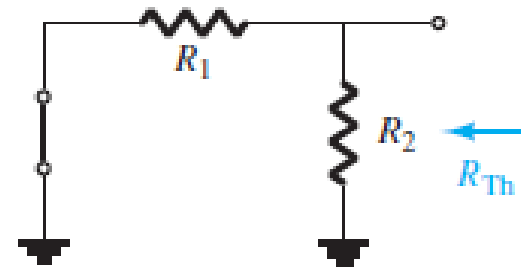
$$R_{TH} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$





# Voltage Divider Bias Circuit

Hence the BE loop can be redrawn as

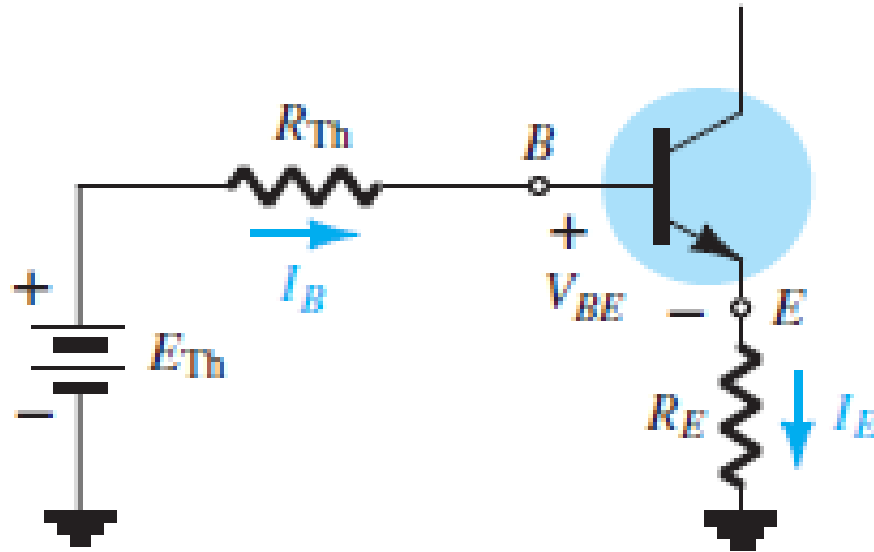

# Voltage Divider Bias Circuit

Now by KVL in this BE loop, we have

$$E_{TH} - I_B \cdot R_{TH} - V_{BE} - I_E \cdot R_E = 0$$

$$\Rightarrow E_{TH} - V_{BE} - I_B R_{TH} - (\beta + 1) I_B R_E = 0$$

$$\Rightarrow E_{TH} - V_{BE} = I_B [R_{TH} + (\beta + 1) R_E]$$

$$\Rightarrow I_B = \frac{E_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

$$\text{Now } I_C = \beta I_B$$

# Voltage Divider Bias Circuit

Now by KVL in this CE loop, we have

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

Substituting  $I_E \approx I_C$

$$V_{CE} = V_{CC} - I_C R_C - I_C R_E$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = V_C - V_E \text{ \& } V_E = I_E R_E$$

$$V_C = V_{CE} + V_E$$

$$V_B = V_{BE} + V_E$$

# Load Line Analysis – Voltage Divider

## Bias Circuit

The CE loop of the fixed bias circuit:


By KVL:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Let  $I_C = 0$ , So  $V_{CE} = V_{CC}$

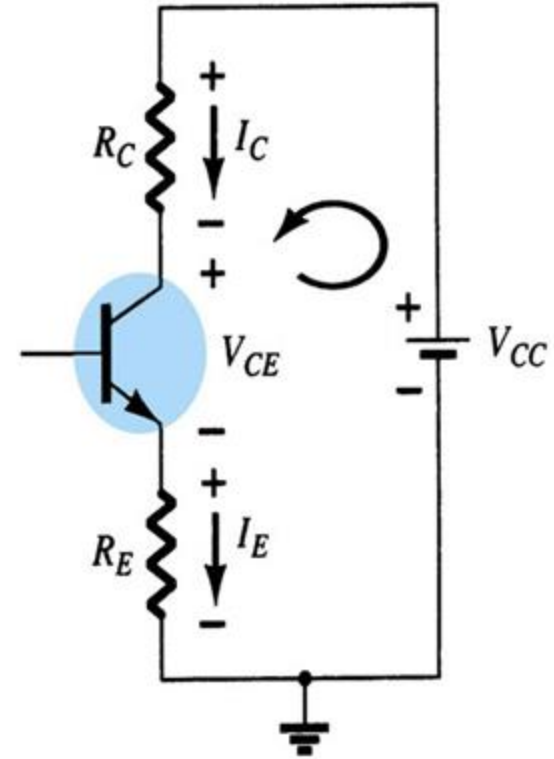
Again, let  $V_{CE} = 0$ , So  $I_C = V_{CC} / (R_C + R_E)$



# Voltage Divider Bias Circuit
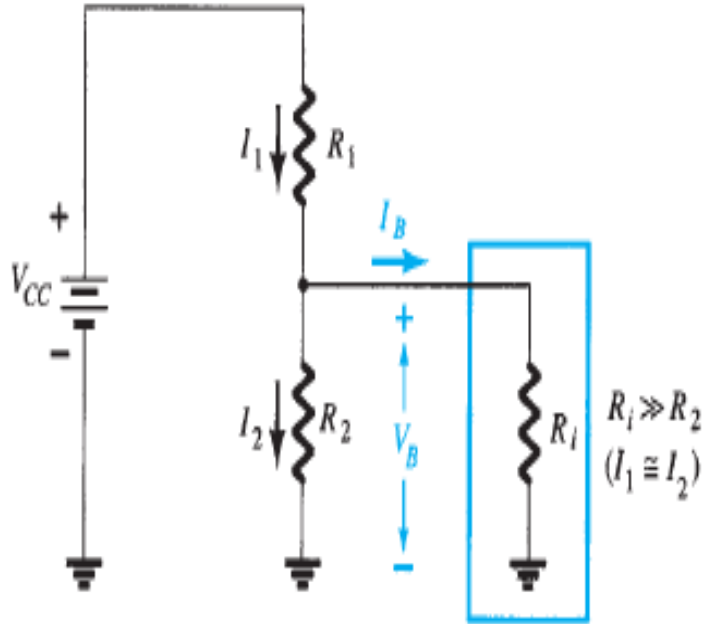
## Approximate Analysis: ( $\beta R_E \geq 10R_2$ )

The input section of the voltage divider configuration can be represented by



$R_i$  is the equivalent resistance between base & ground for the transistor with emitter resistance  $R_E$ .

Assuming  $R_i \gg R_E$ , we have  $I_B = 0$ . Hence  $I_1 = I_2$  and  $R_1$  &  $R_2$  can be considered as series.

# Voltage Divider Bias Circuit

So by voltage division rule, the voltage across  $R_2$  which is the base voltage is given by

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Since  $R_i = (\beta + 1) R_E \approx \beta R_E$ , the condition for this analysis can be chosen as  $\beta R_E \geq 10 R_2$ .

Now  $V_E = V_B - V_{BE}$

The emitter current can be determined as,

$$I_E = \frac{V_E}{R_E}$$

and,  $I_C \approx I_E$

# Voltage Divider Bias Circuit

Now by applying KVL in CE loop

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$


PRACTICE




# Voltage Divider Bias Circuit

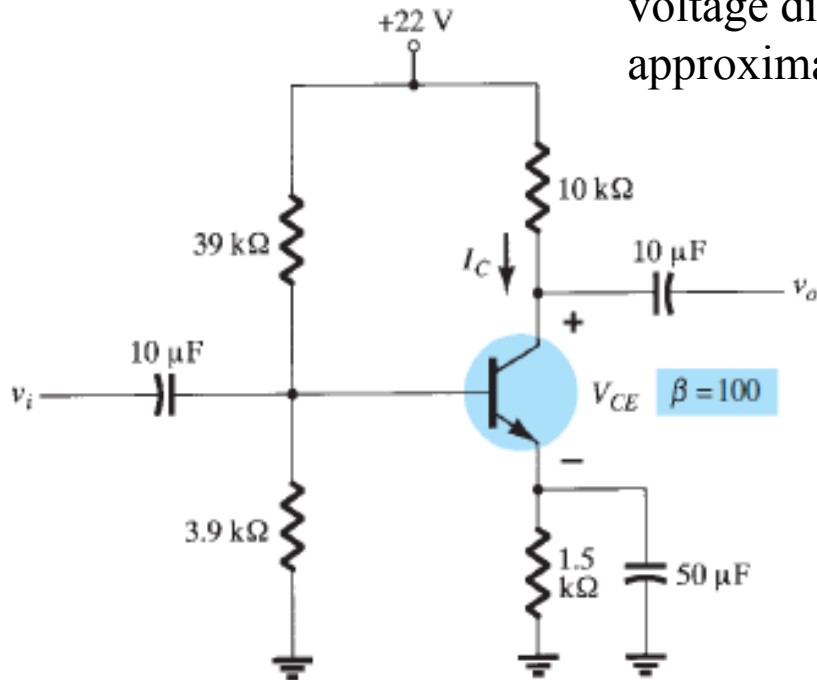Example:

Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for the voltage divider configuration using exact analysis & approximate analysis.



# DC Bias with Voltage Feedback:

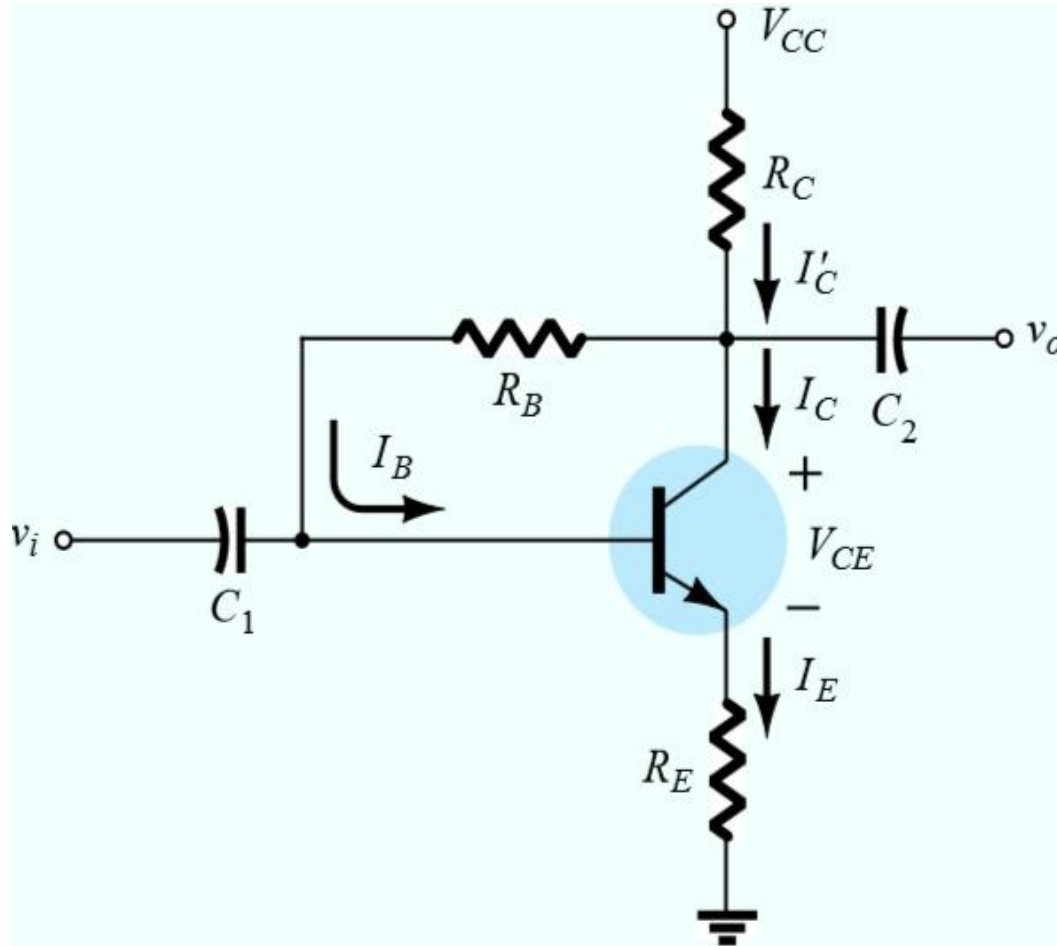


Here  $I'_C = I_B + I_C$

The actual value of  $I_C$  &  $I'_C$  far exceeds the value of  $I_B$ .

Hence we can say that,

$$I'_C \approx I_C$$

# DC Bias with Voltage Feedback:

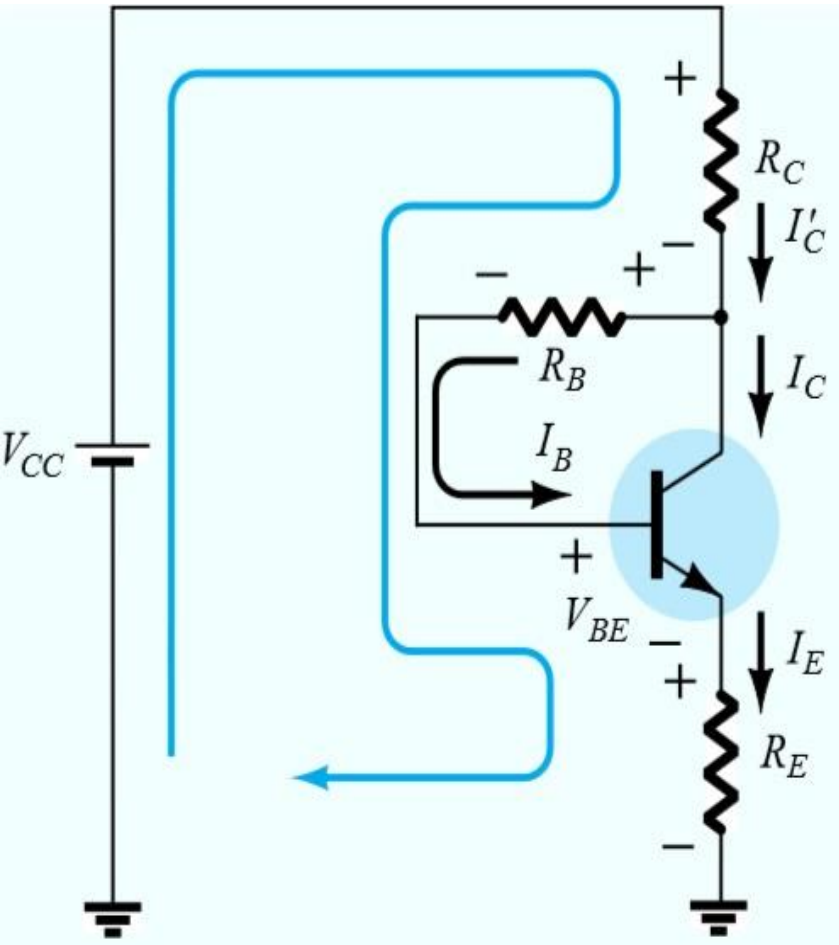


Applying KVL in BE loop,

$$\begin{aligned} V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E &= 0 \\ \Rightarrow V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E &= 0 \\ \Rightarrow V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - & \\ (\beta + 1) I_B R_E &= 0 \end{aligned}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C + (\beta + 1) R_E}$$

# DC Bias with Voltage Feedback:

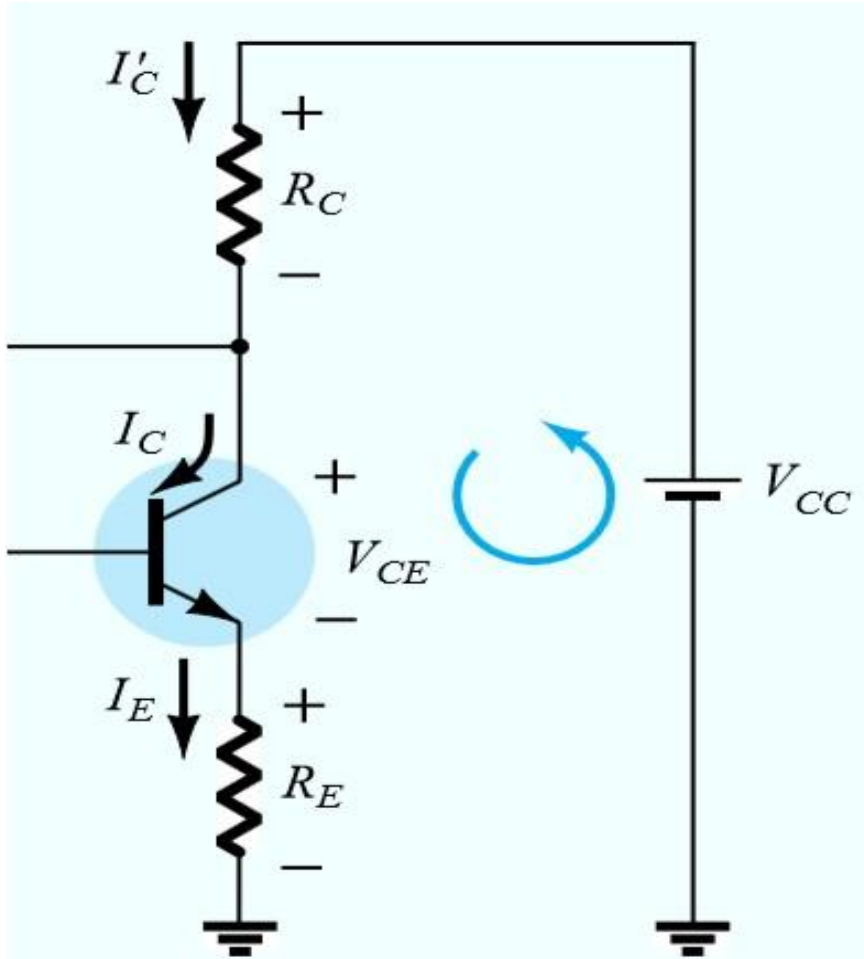

Applying KVL in CE loop,

$$V_{CC} - I'_C R_C - V_{CE} - I_E R_E = 0$$


$$\Rightarrow V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\Rightarrow V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$

PRACTICE

# DC Bias with Voltage Feedback:

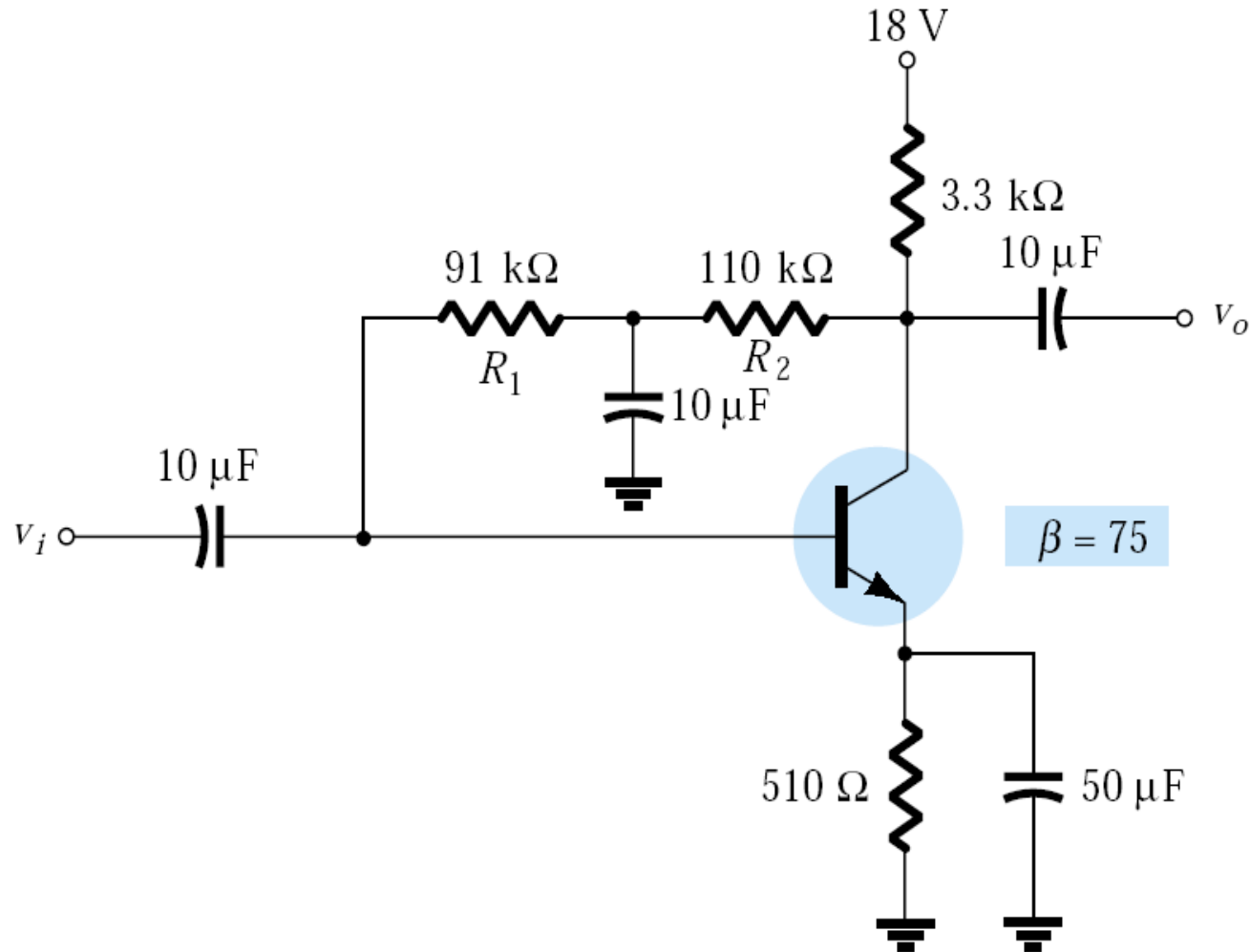

Determine:

- a)  $I_B$
- b)  $I_C$
- c)  $V_{CE}$
- d)  $V_E$
- e)  $V_C$